
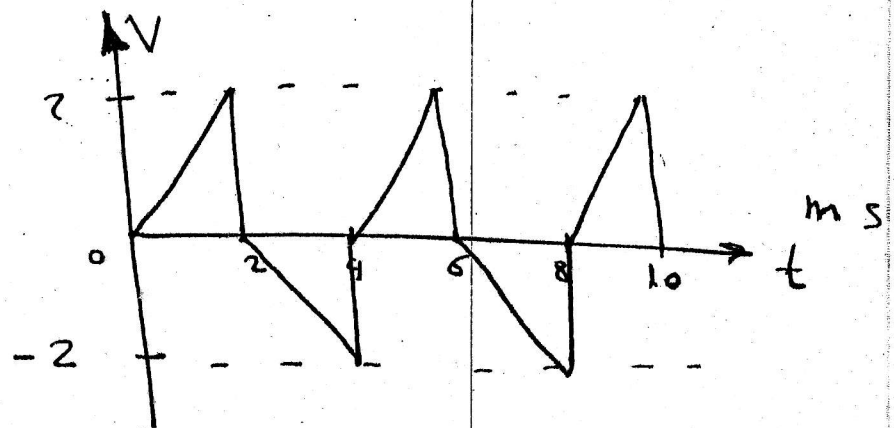


2009

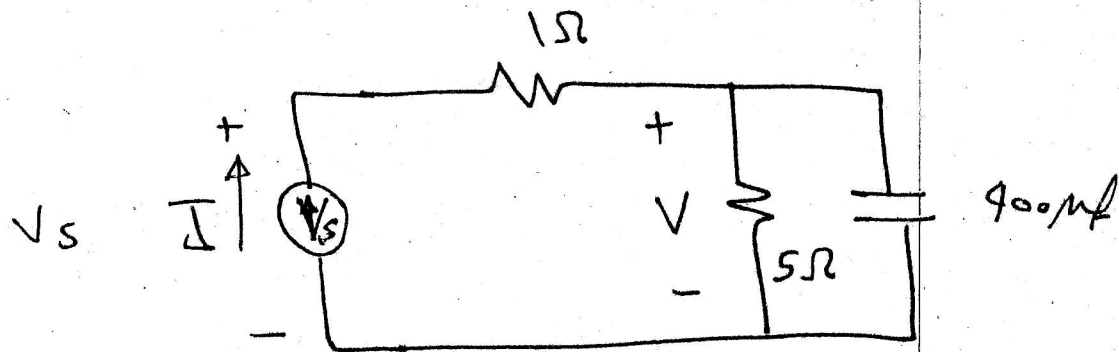

$$V = \begin{cases} t & 0 \leq t \leq 2 \\ -t + C_1 & 2 \leq t \leq 4 \\ t + C_2 & 4 \leq t \leq 6 \\ -t + C_3 & 6 \leq t \leq 8 \\ t + C_4 & 8 \leq t \leq 10 \end{cases}$$

$$V = -t + C_1 \quad 0 \leq t \leq 2$$

$$V(2) = 0 = -2 + C_1 \rightarrow C_1 = 2$$

$$V = t + C_2$$

$$V(4) = 0 = 4 + C_2 \rightarrow C_2 = -4$$

$$V = -t + C_3$$

$$6 \leq t \leq 8$$

$$V(6) = 0 = -6 + C_3 \rightarrow C_3 = 6$$

$$V = t + C_4$$

$$8 \leq t \leq 10$$

$$V(8) = 0 = 8 + C_4 \rightarrow C_4 = -8$$

$$\therefore V =$$

$$\left\{ \begin{array}{l} t \\ -t + 2 \\ t - 4 \\ -t + 6 \\ t - 8 \end{array} \right.$$

$$0 \leq t \leq 2$$

$$2 \leq t \leq 4$$

$$4 \leq t \leq 6$$

$$6 \leq t \leq 8$$


$$8 \leq t \leq 10$$

$$\therefore I = I'_R + I'_C$$

$$= \frac{V}{R} + C \frac{dV}{dt}$$

$$\therefore V_S = I \times 1\Omega + V$$

2

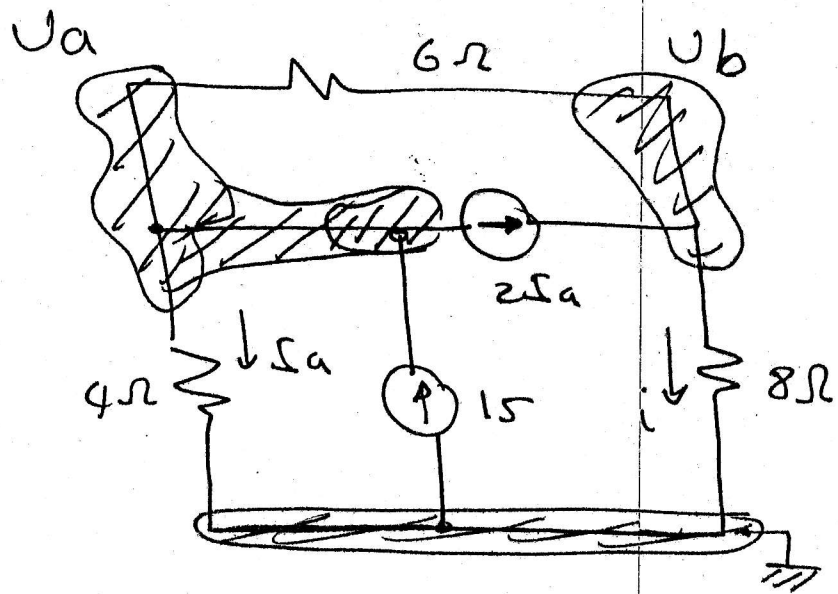

3

① Node methode

at node Va

$$15 - 2I_a = \frac{V_a - V_b}{6} + \frac{V_a - 0}{4}$$

at Vb

$$2I_a = \frac{V_b - V_a}{6} + \frac{V_b - 0}{8}$$


$$I_a = \frac{V_a}{4}$$

بدل V_a و V_b در معادله

$$I = \frac{V_b}{8}$$

ع

دست

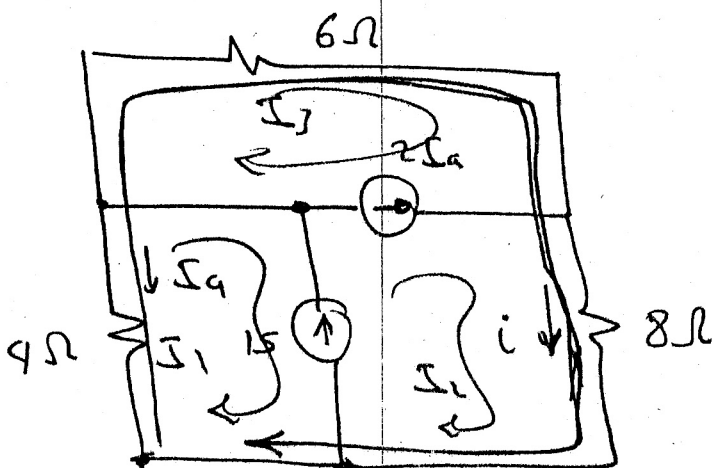

→ ①



سنتز فکره

مركز التعليم والتدريب
شماره تماس: ۰۱۰۰۶۲۶۸۵۸ - ۰۱۴۲۰۰۶۲۲۲

$$I_3$$

$$-I_3$$


$$+I_2 = I_3$$

→ ②


$$-I_1$$

$$+6I_3 + 8I_2$$
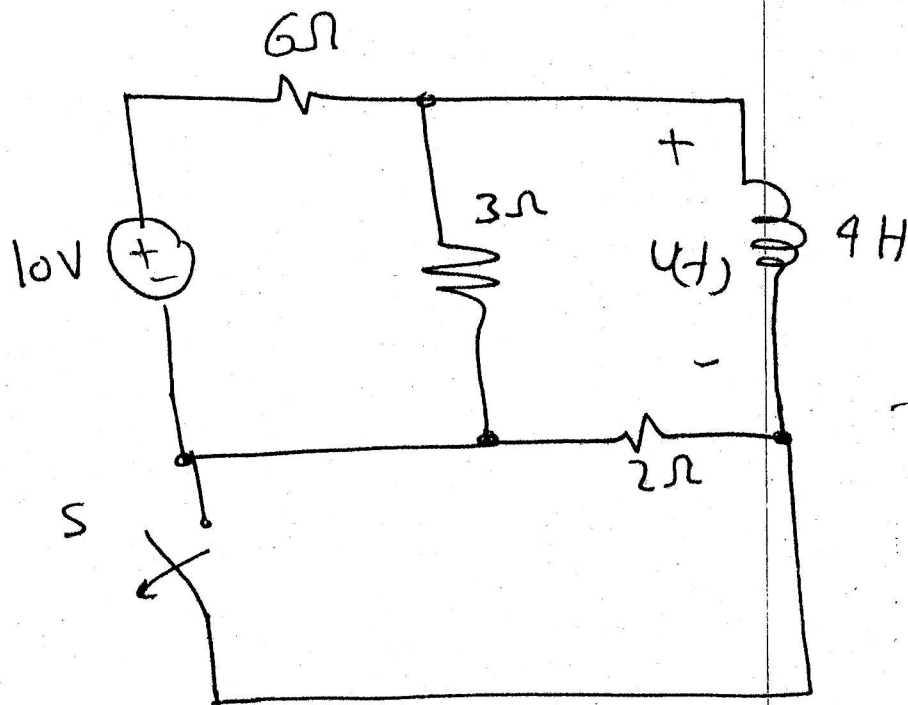
$$\text{حل لاجزای ۱، ۲، ۳، ۴} \rightarrow ④$$









if $S \rightarrow \text{Closed}$

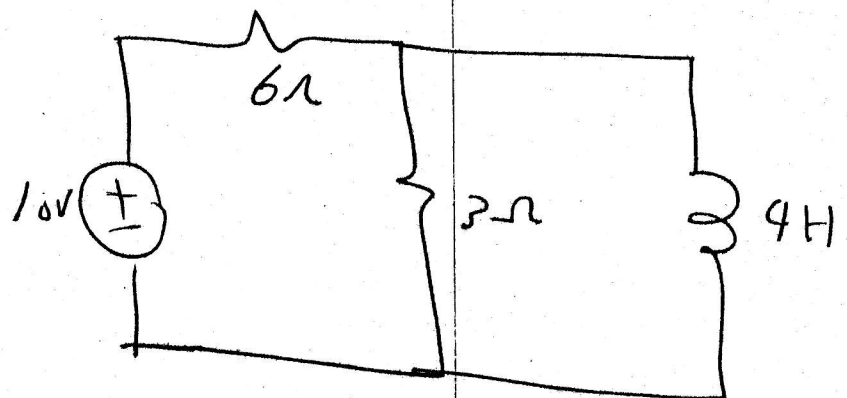

$$v(\infty) = 0$$

$$i(\infty) = \frac{10}{6}$$

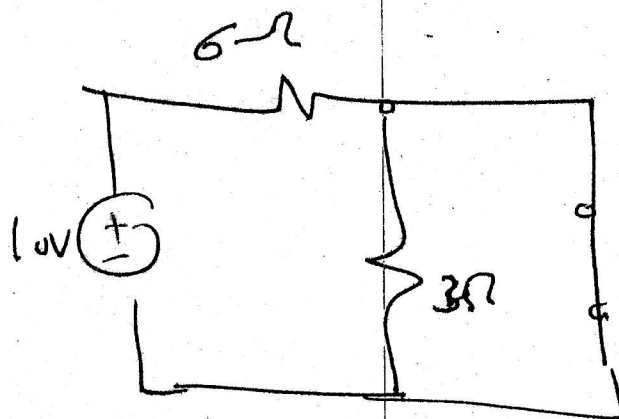

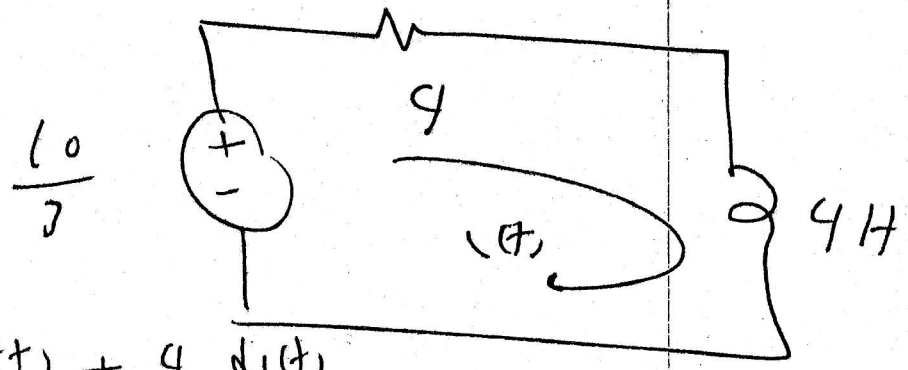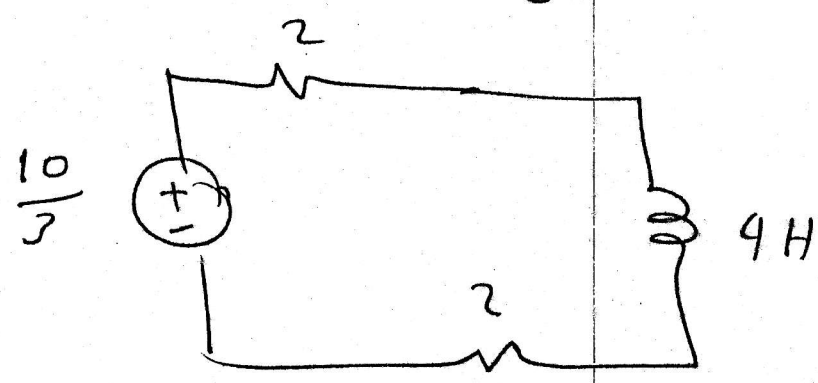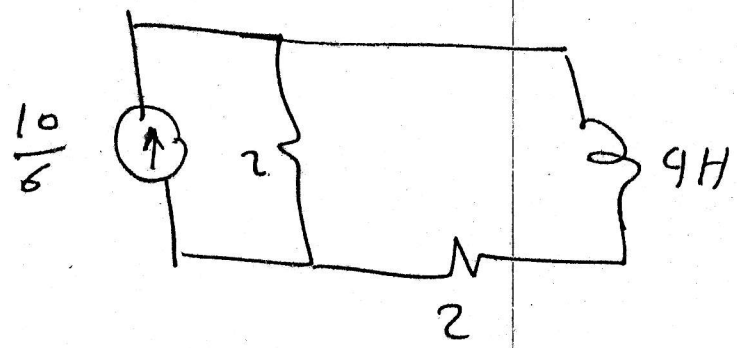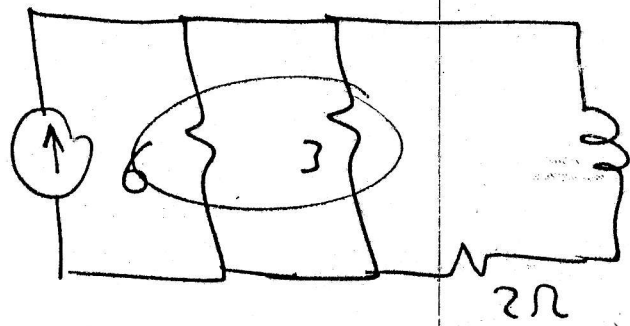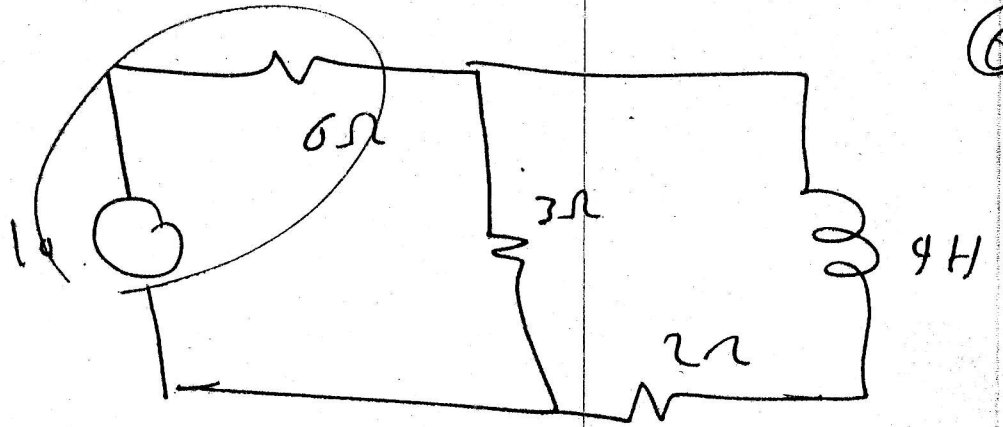

$$\frac{10}{3} = 4 i(t) + 4 \frac{di(t)}{dt}$$

$$\frac{10}{12} = i(t) + \frac{di(t)}{dt}$$

$$i_c(t) = k e^{-at}$$

$$= k e^{-t}$$

$$i_p(t) = A$$

$$\frac{10}{12} = A + 0$$

$$A = \frac{10}{12}$$

$$i(t) = i_c(t) + i_p(t)$$


$$= k e^{-t} + \frac{10}{12}$$

$$i(0) = \frac{10}{6} = k + \frac{10}{12}$$


$$k = \frac{10}{6} - \frac{10}{12}$$

$$\therefore i(t) = \text{_____}$$
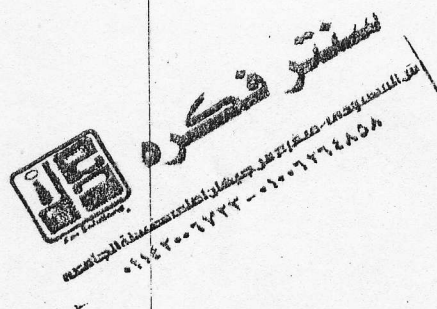
$$i(t) = L \frac{di(t)}{dt} + \gamma \frac{di(t)}{dt}$$



Q

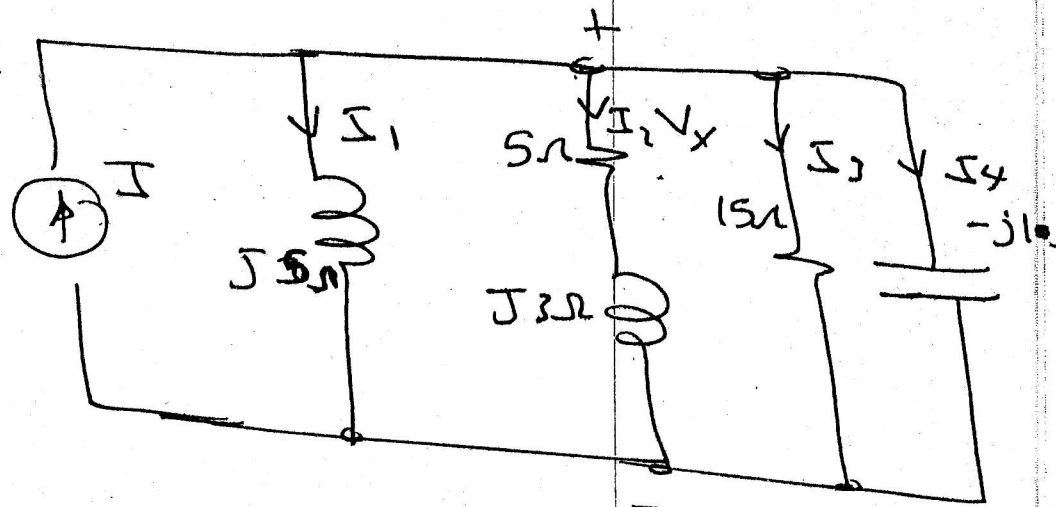

$$P_{5\Omega} = 500 \text{ watt}$$

$$P_5 = \frac{V^2}{R} = 500 = \frac{V^2}{5\Omega} \rightarrow V^2 = 2500$$

$$\therefore P_{5\Omega} = I_2^2 \cdot R = 500 = I_2^2 \times 5 \quad I_2^2 = \frac{500}{5}$$

$$\therefore I_2 = 10 \text{ A}$$

$$\therefore V_x = I_2 \times 5 + j3$$

$$V_x = 10 (5 + j3)$$

$$= 50 + j30$$

$$\frac{1}{Z_T} = \frac{1}{5\Omega} + \frac{1}{5+j3} + \frac{1}{15} + \frac{1}{-j10}$$


$$\therefore Z_T = \checkmark$$

$$I = \frac{V_x}{Z_T}$$


$$P.f = \cos \theta_z$$

Using Superposition Find $v(t)$


9

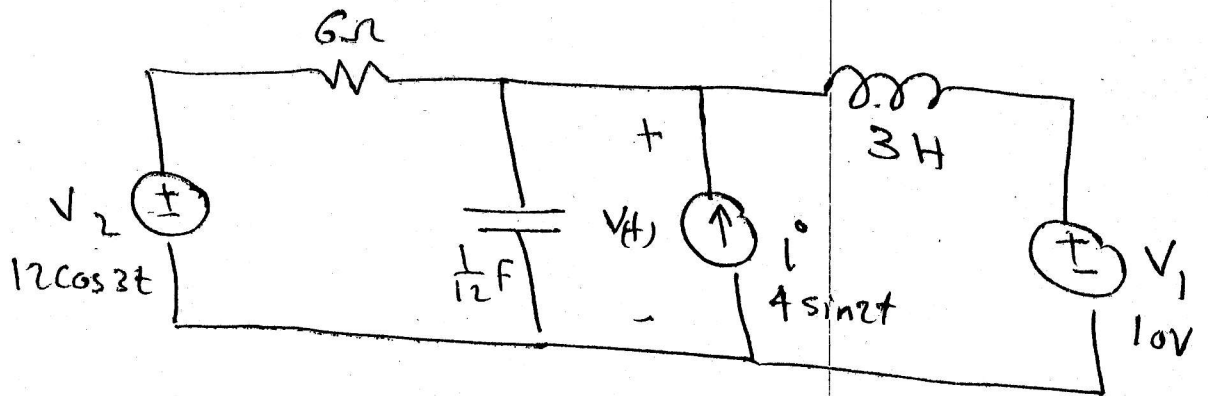

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

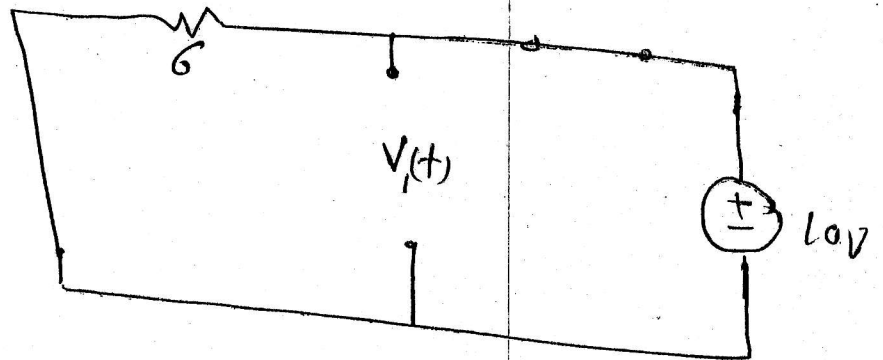



$$v_1(t) = 10V$$

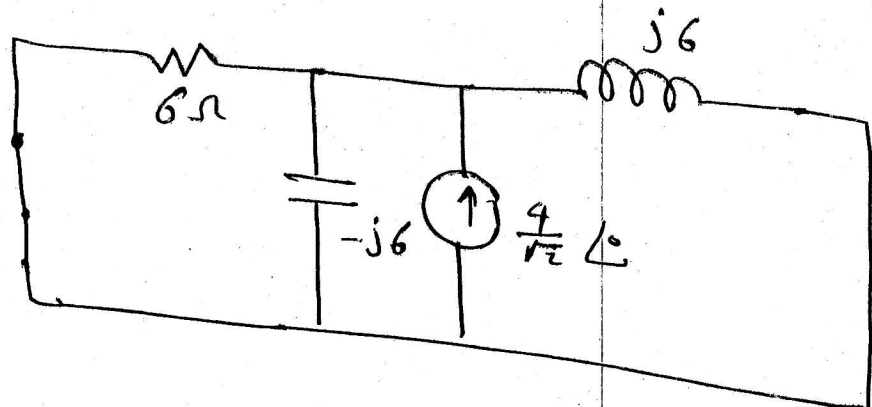

$$v_2(t) = \frac{4}{\sqrt{2}} \angle 0^\circ \times 6$$

$$= \frac{24}{\sqrt{2}} \angle 0^\circ$$

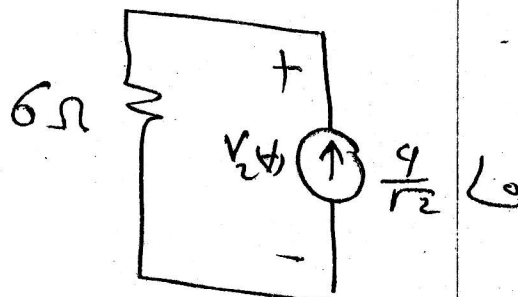

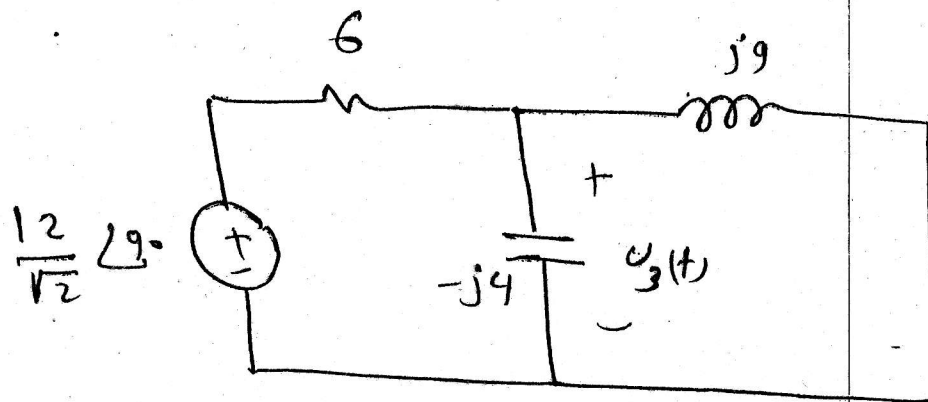


$$V_3(t) = \frac{12}{\sqrt{2}} \angle 90^\circ * \frac{((j9 * (-j4)) / (j9 - j4))}{6 + \left(\frac{j9 * -j4}{j5} \right)}$$


$$\therefore V(t) = V_1(t) + V_2(t) + V_3(t)$$


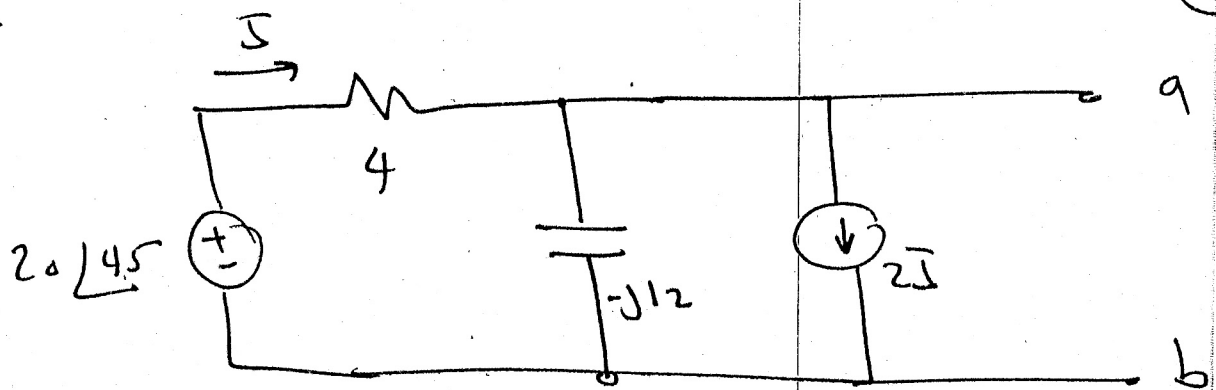
$$P_{6\Omega} = \frac{V^2}{R} = \frac{(V_2 - V(t))^2}{6\Omega}$$



To find V_{th}

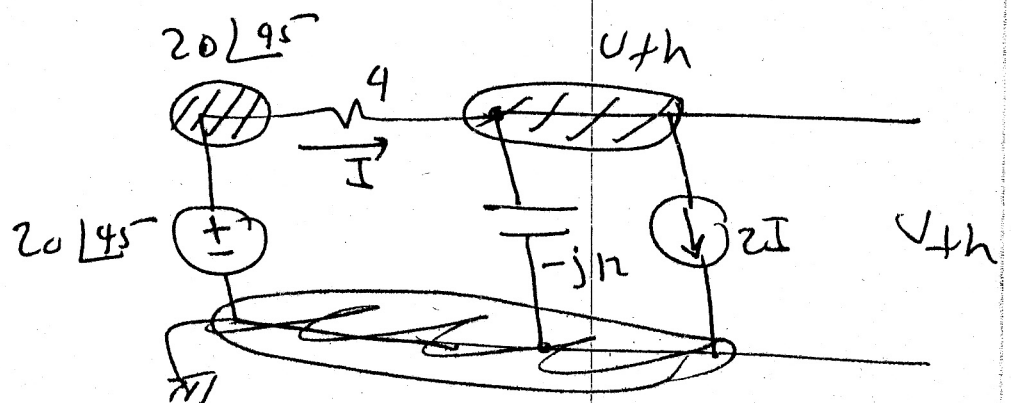


K.C.L at V_{th}

$$\frac{V_{th} - 20\angle 45^\circ}{4} + \frac{V_{th} - 0}{-j12} = -2I$$

$$\therefore I = 20\angle 45^\circ - V_{th}$$

$$\therefore \frac{V_{th} - 20\angle 45^\circ}{4} + \frac{V_{th} - 0}{-j12} = -2(20\angle 45^\circ - V_{th})$$
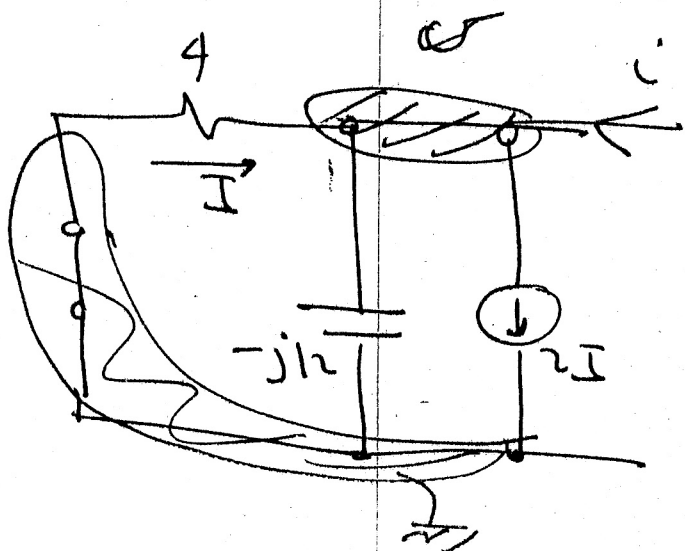
$$\therefore V_{th} = \underline{\hspace{2cm}}$$



$$0 + \frac{V - 0}{-j12}$$

→ ①

$$= -\frac{V}{4}$$

→ ②

$$\frac{V}{4} + j\frac{V}{12}$$

$$\left(\frac{1}{4} + \frac{j}{12} - \frac{1}{2} \right)$$

1

$$\left(\frac{1}{4} + \frac{j}{12} - \frac{1}{2} \right)$$


$$\angle \theta_R \rightarrow R = |L|$$

4 Real ZL


7


$$Z = 30 \angle 30^\circ$$

$$V_L = 208$$

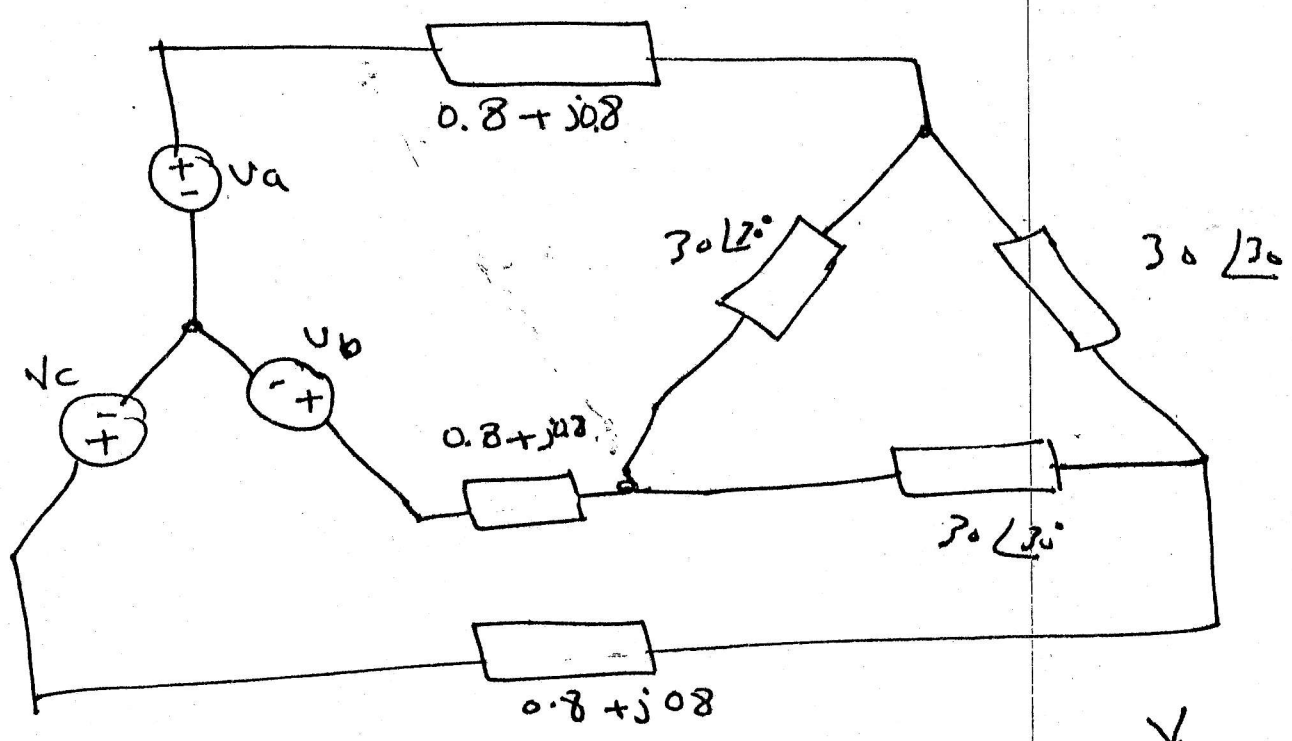

$Y \leftarrow \Delta Y \Delta$

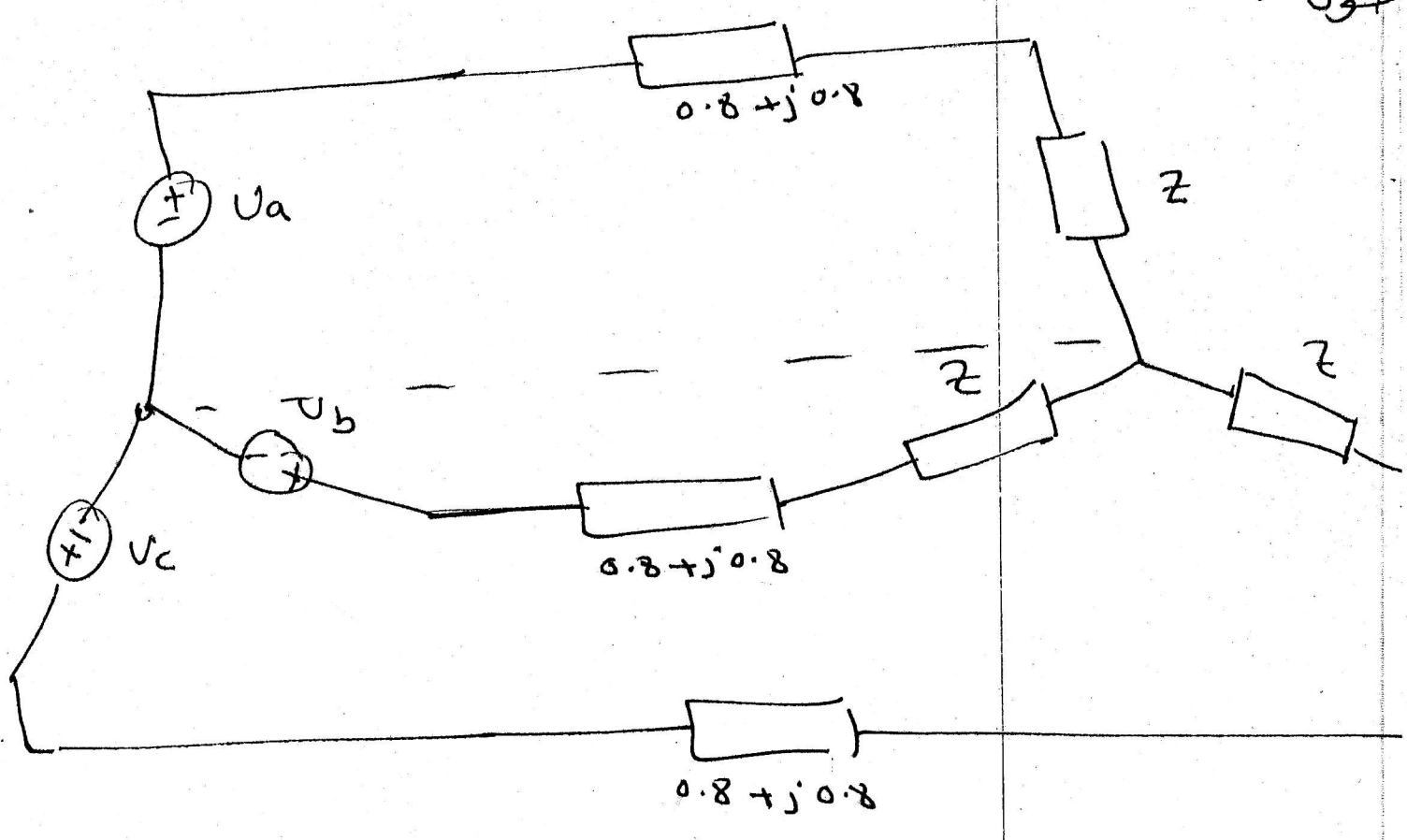

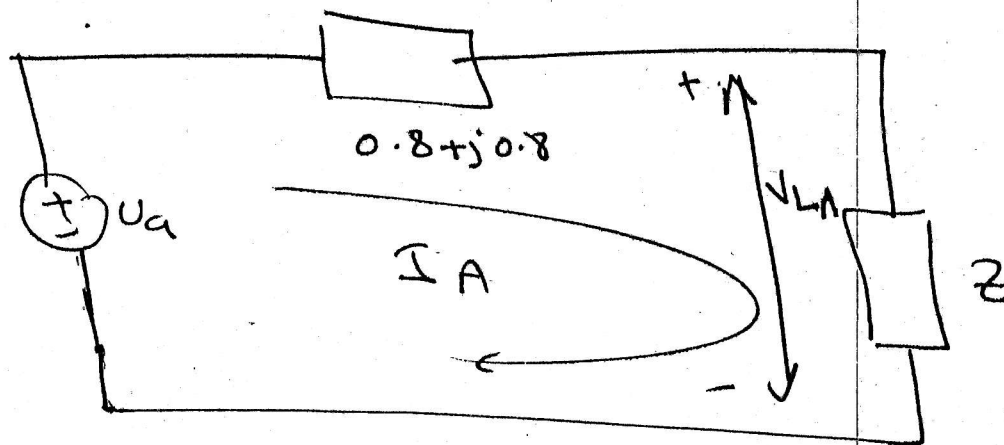

$$U_a = \frac{208}{\sqrt{3}} \angle 0^\circ$$

$$\therefore I_A = \left(\frac{208 \angle 0^\circ}{\sqrt{3}} \right) / (0.8 + j0.8 + Z)$$

$$-U_a + I_A(0.8 + j0.8) + V_{LA}$$

$$V_{LA} = U_a - I_A(0.8 + j0.8)$$

حل باقی تنہا لکھو